

---

## **Week 6**


# **The 8088 and 8086 Microprocessors and Their Memory and Input/Output Interfaces**

# 8086 and 8088 Microprocessors

---

- 8086 announced in 1978; 8086 is a 16 bit microprocessor with a 16 bit data bus
- 8088 announced in 1979; 8088 is a 16 bit microprocessor with an 8 bit data bus
- Both manufactured using High-performance Metal Oxide Semiconductor (HMOS) technology
- Both contain about 29000 transistors
- Both are packaged in 40 pin dual-in-line package (DIP)
- Address lines A0-A7 and Data lines D0-D7 are multiplexed in 8088
  - By multiplexed we mean that the same physical pin carries an address bit at one time and the data bit another time
- Address lines A0-A15 and Data lines D0-D15 are multiplexed in 8086

# 8088 and 8086 Microprocessors

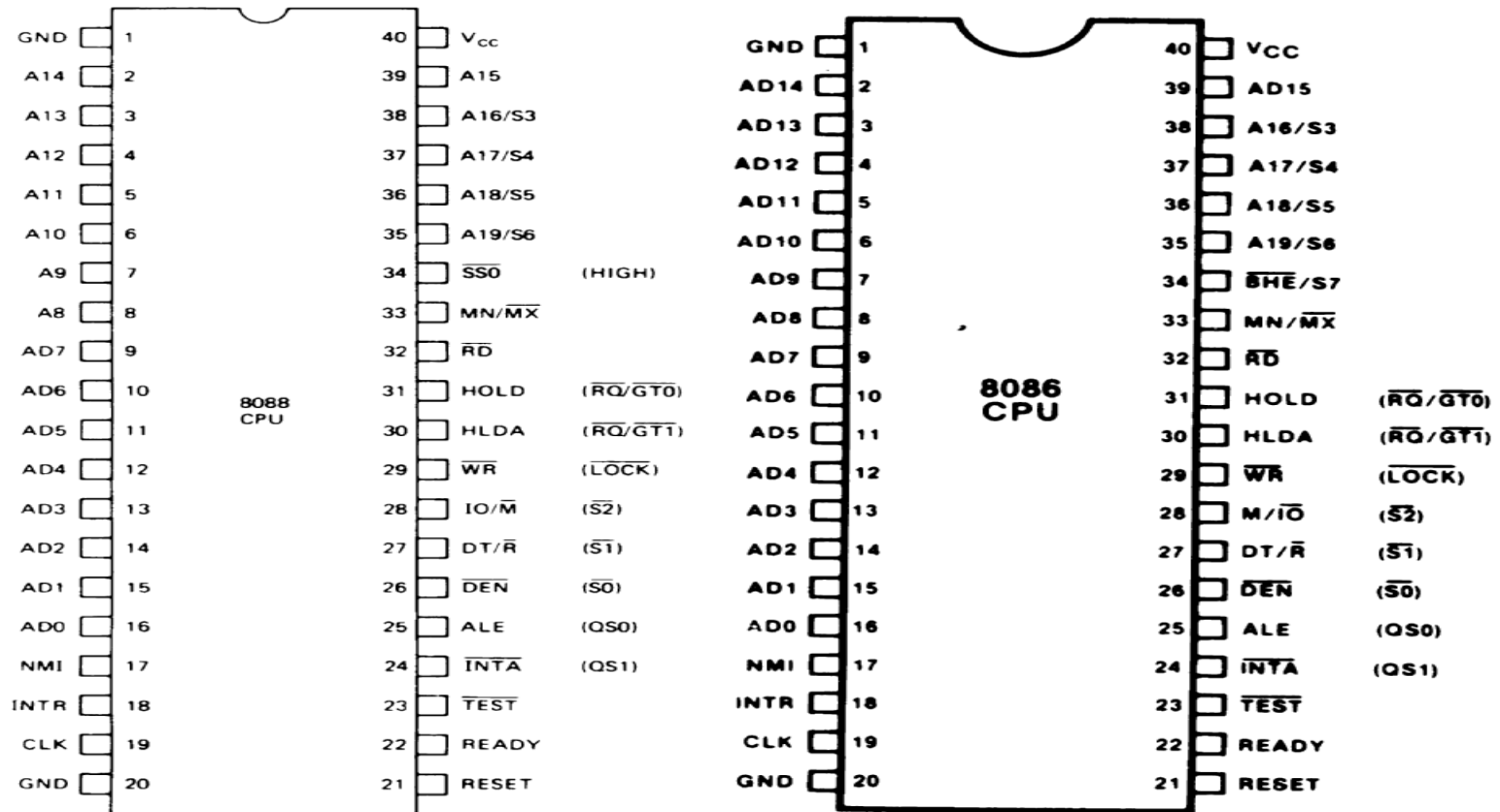

# Minimum-mode and Maximum-mode Systems

---

- 8088 and 8086 microprocessors can be configured to work in either of the two modes: the minimum mode and the maximum mode
- Minimum mode:
  - Pull MN/**MX** to logic 1
  - Typically smaller systems and contains a single microprocessor
- Maximum mode
  - Pull MN/**MX** logic 0
  - Larger systems with more than one processor

# Minimum-mode and Maximum-mode Systems

---

Signals common to both minimum and maximum systems

Common signals		
Name	Function	Type
AD7-AD0	Address/data bus	Bidirectional, 3-state
A15-A8	Address bus	Output, 3-state
A19/S6-A16/S3	Address/status	Output, 3-state
MN/ $\overline{\text{MX}}$	Minimum/maximum Mode control	Input
$\overline{\text{RD}}$	Read control	Output, 3-state
$\overline{\text{TEST}}$	Wait on test control	Input
READY	Wait state control	Input
RESET	System reset	Input
NMI	Nonmaskable Interrupt request	Input
INTR	Interrupt request	Input
CLK	System clock	Input
V <sub>cc</sub>	+5 V	Input
GND	Ground	

# Minimum-mode and Maximum-mode Systems

---

Minimum mode signals ( $MN/\overline{MX} = V_{CC}$ )		
Name	Function	Type
HOLD	Hold request	Input
HLDA	Hold acknowledge	Output
$\overline{WR}$	Write control	Output, 3-state
$IO/\overline{M}$	IO/memory control	Output, 3-state
$DT/\overline{R}$	Data transmit/receive	Output, 3-state
$\overline{DEN}$	Data enable	Output, 3-state
$\overline{SSO}$	Status line	Output, 3-state
ALE	Address latch enable	Output
$\overline{INTA}$	Interrupt acknowledge	Output

Minimum mode unique signals


# Minimum-mode and Maximum-mode Systems

---

<b>Maximum mode signals (<math>\overline{MN}/\overline{MX} = \text{GND}</math>)</b>		
<b>Name</b>	<b>Function</b>	<b>Type</b>
$\overline{RQ}/\overline{GT1}, 0$	Request/grant bus access control	Bidirectional
$\overline{LOCK}$	Bus priority lock control	Output, 3-state
$\overline{S2}-\overline{S0}$	Bus cycle status	Output, 3-state
$QS1, QS0$	Instruction queue status	Output


**Maximum mode unique signals**

# 8088 Minimum-mode block diagram

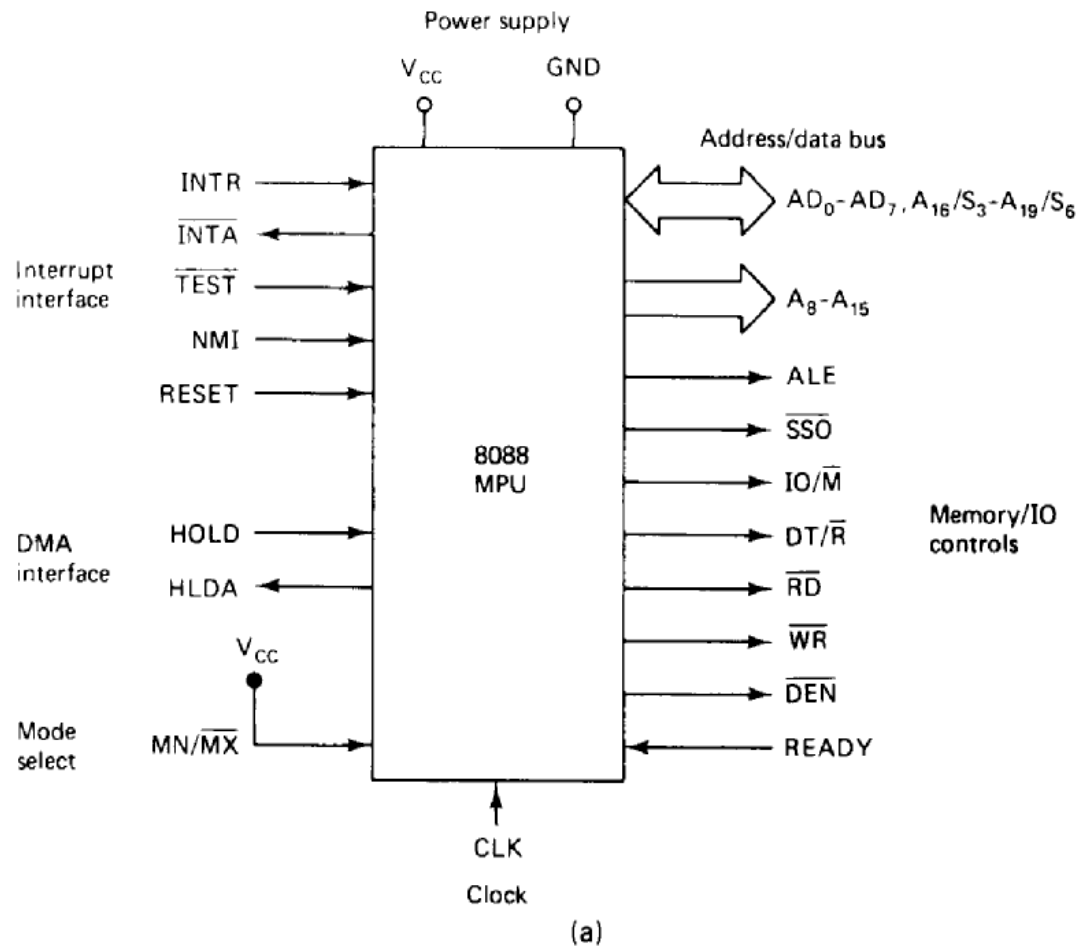



# 8086 Minimum-mode block diagram

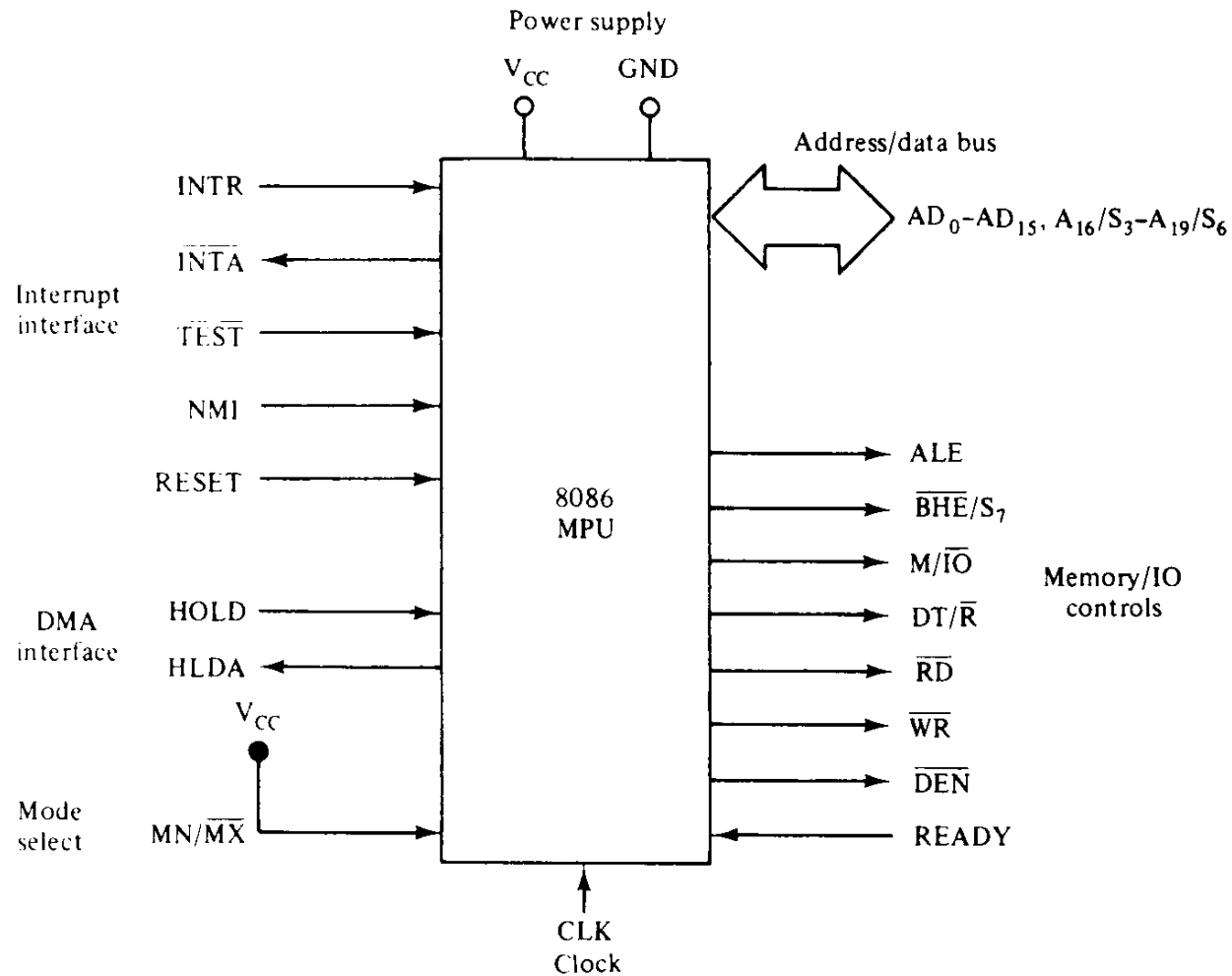

# Minimum Mode Interface

---

- Address/Data bus: 20 bits vs 8 bits multiplexed
- Status signals:  $A_{16}$ - $A_{19}$  multiplexed with status signals  $S_3$ - $S_6$  respectively
  - $S_3$  and  $S_4$  together form a 2 bit binary code that identifies which of the internal segment registers was used to generate the physical address that was output on the address bus during the current bus cycle.
  - $S_5$  is the logic level of the internal interrupt enable flag,  $s_6$  is always logic 0.

S4	S3	Address status
0	0	Alternate (relative to ES segment)
0	1	Stack (relative to SS Segment)
1	0	Code/None (relative to CS segment or a default zero)
1	1	Data (relative to DS segment)

# Minimum Mode Interface

---

- Control Signals: (8088)
  - **Address Latch Enable (ALE)** is a pulse to logic 1 that signals external circuitry when a valid address is on the bus. This address can be latched in external circuitry on the 1-to-0 edge of the pulse at ALE.
  - **$\overline{\text{IO/M}}$  line:** memory or I/O transfer is selected (complement for 8086)
  - **$\overline{\text{DT/R}}$  line:** direction of data is selected
  - **SSO (System Status Output) line:** =1 when data is read from memory and =0 when code is read from memory (only for 8088)
  - **$\overline{\text{BHE}}$  (Bank High Enable) line :** =0 for most significant byte of data for 8086 and also carries  $S_7$
  - **$\overline{\text{RD}}$  line:** =0 when a read cycle is in progress
  - **$\overline{\text{WR}}$  line:** =0 when a write cycle is in progress
  - **$\overline{\text{DEN}}$  line: (Data enable)** Enables the external devices to supply data to the processor.
  - **Ready line:** can be used to insert wait states into the bus cycle so that it is extended by a number of clock periods.

# Minimum Mode Interface

---


- Interrupt signals:
  - INTR (Interrupt request) :=1 shows there is a service request, sampled at the final clock cycle of each instruction acquisition cycle.
  - **INTA** : Processor responds with two pulses going to 0 when it services the interrupt and waits for the interrupt service number after the second pulse.
  - **TEST**: Processor suspends operation when =1. Resumes operation when=0. Used to synchronize the processor to external events.
  - NMI (Nonmaskable interrupt) : A leading edge transition causes the processor go to the interrupt routine after the current instruction is executed.
  - RESET : =0 Starts the reset sequence.

# Minimum Mode Interface

---


- DMA (Direct Memory Access) Interface Signals:
  - HOLD : External device puts logic level 1 to HOLD input to take control of the bus for DMA request.
  - HLDA (Hold acknowledge) : Processor responds by putting logic level 1 to HDLA.
  - In this state; Address and Data lines,  $\overline{SSO}$ ,  $\overline{IO/\overline{M}}$ ,  $\overline{DT/R}$ ,  $\overline{RD}$ ,  $\overline{WR}$ ,  $\overline{DEN}$  signals are all put to high-Z state.
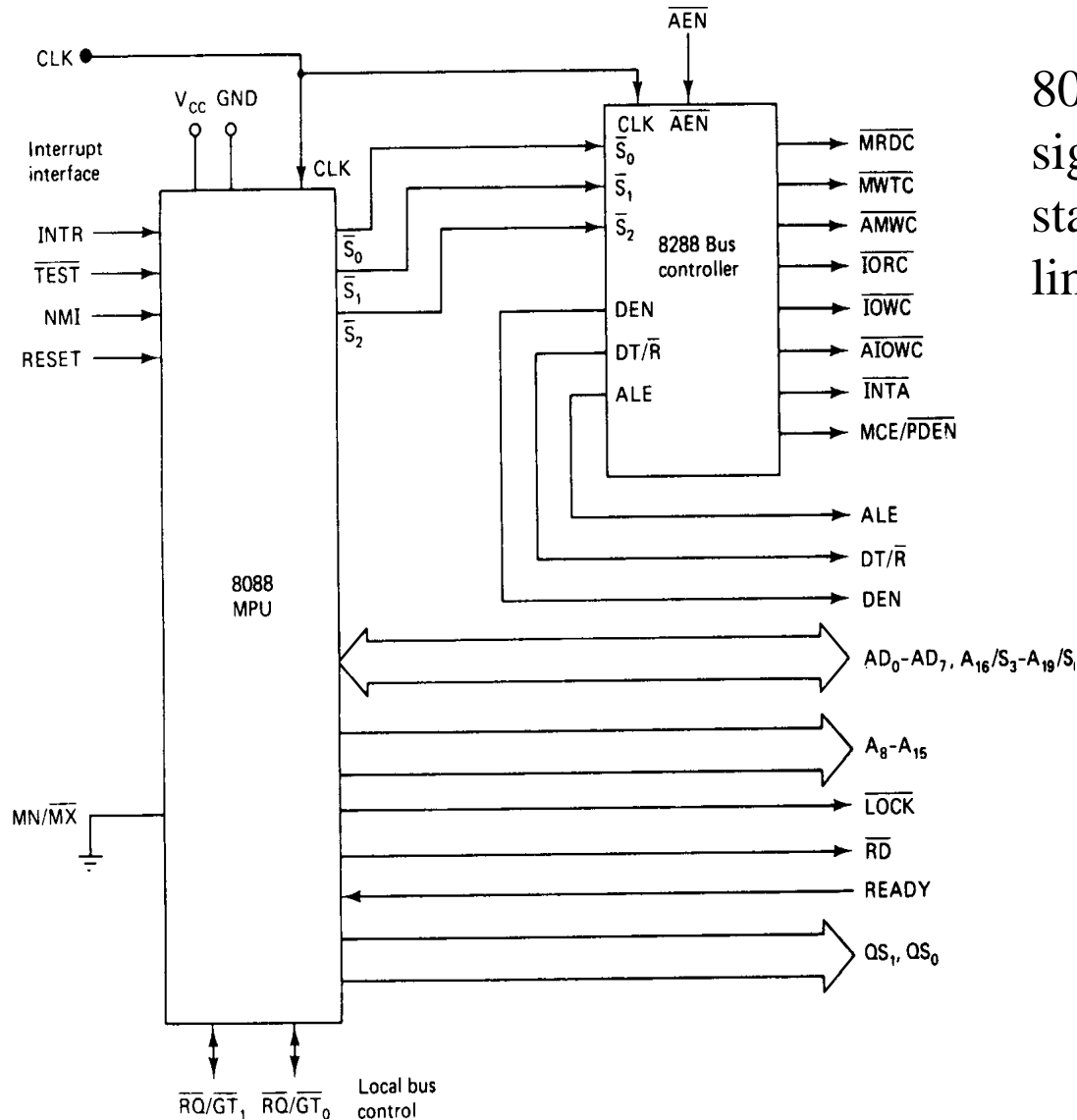
# Maximum-mode interface circuit diagram (8088)



8088 does not provide all the signals, instead it outputs a status code on three signal lines S0, S1, and S2
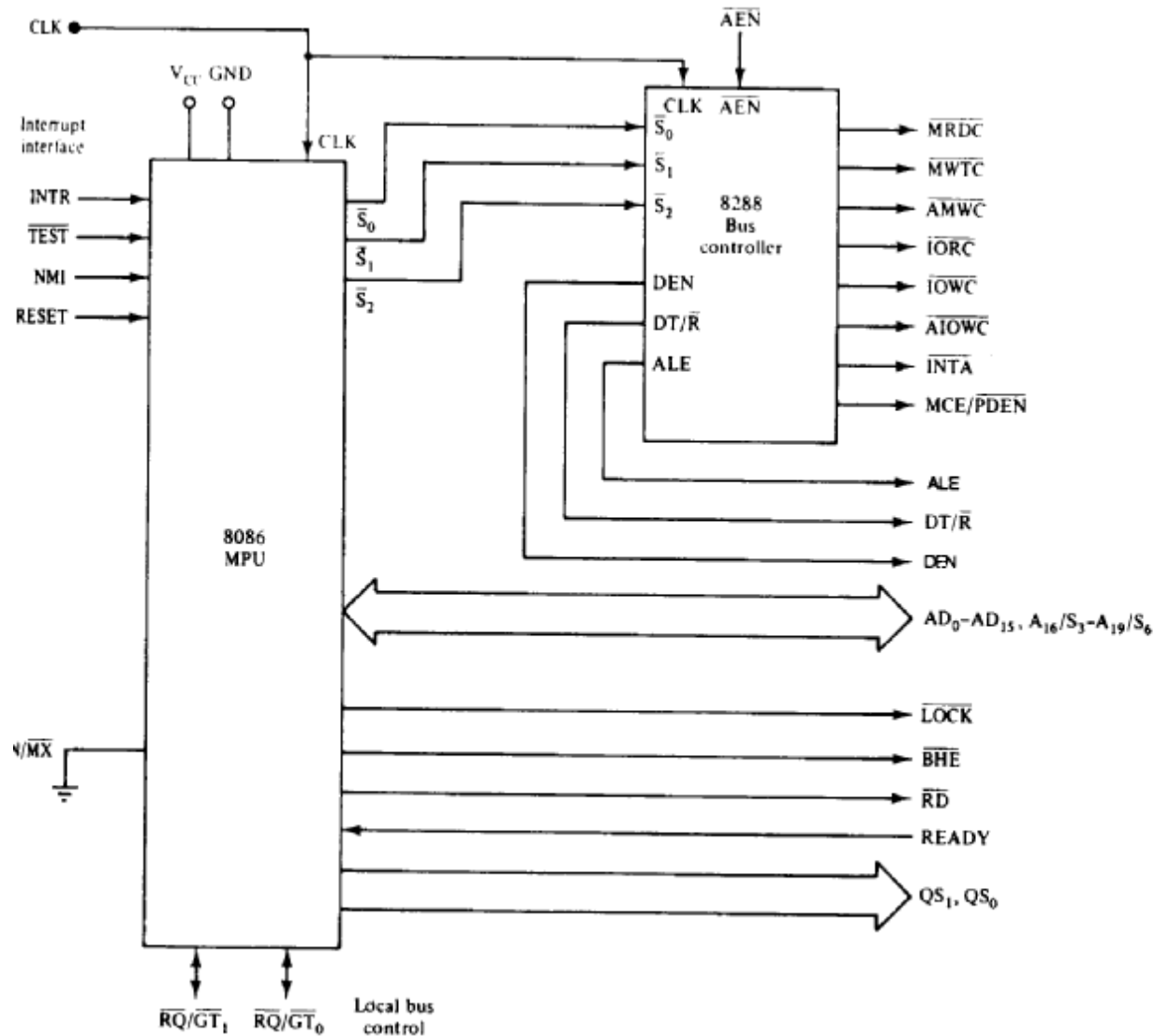
# Maximum-mode interface circuit diagram (8086)



# Maximum Mode Interface

---

- For multiprocessor environment
- 8288 Bus Controller is used for bus control
- $WR^-$ ,  $IO/M^-$ ,  $DT/R^-$ ,  $DEN^-$ ,  $ALE$ ,  $INTA^-$  signals are not available
- Instead:
  - **$MRDC^-$**  (memory read command)
  - **$MWRT^-$**  (memory write command)
  - **$AMWC^-$**  (advanced memory write command)
  - **$IORC^-$**  (I/O read command)
  - **$IOWC^-$**  (I/O write command)
  - **$AIOWC^-$**  (Advanced I/O write command)
  - **$INTA^-$**  (interrupt acknowledge)



# Status Bits

---

They indicate the function of the current bus cycle. They are normally decoded by the 8288 bus controller


Status Inputs			CPU Cycle	8288 Command
$\overline{S2}$	$\overline{S1}$	$\overline{S0}$		
0	0	0	Interrupt Acknowledge	$\overline{INTA}$
0	0	1	Read I/O Port	$\overline{IORC}$
0	1	0	Write I/O Port	$\overline{IOWC, AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction Fetch	$\overline{MRDC}$
1	0	1	Read Memory	$\overline{MRDC}$
1	1	0	Write Memory	$\overline{MWTC, AMWC}$
1	1	1	Passive	None

# Maximum Mode Interface

---

- The signals shown above are produced by 8288 depending on the state of  $S_0$ ,  $S_1$  and  $S_2$ .
- **DEN**, **DT/R<sup>-</sup>** and **ALE** signals are the same as minimum-mode systems
- **LOCK<sup>-</sup>**: when =0, prevents other processors from using the bus
- **QS<sub>0</sub>** and **QS<sub>1</sub>** (queue status signals) : informs about the status of the queue
- **RQ<sup>-</sup>/GT<sup>-</sup><sub>0</sub>** and **RQ<sup>-</sup>/GT<sup>-</sup><sub>1</sub>** are used instead of **HOLD** and **HLDA** lines in a multiprocessor environment as request/grant lines.

# Maximum Mode Interface

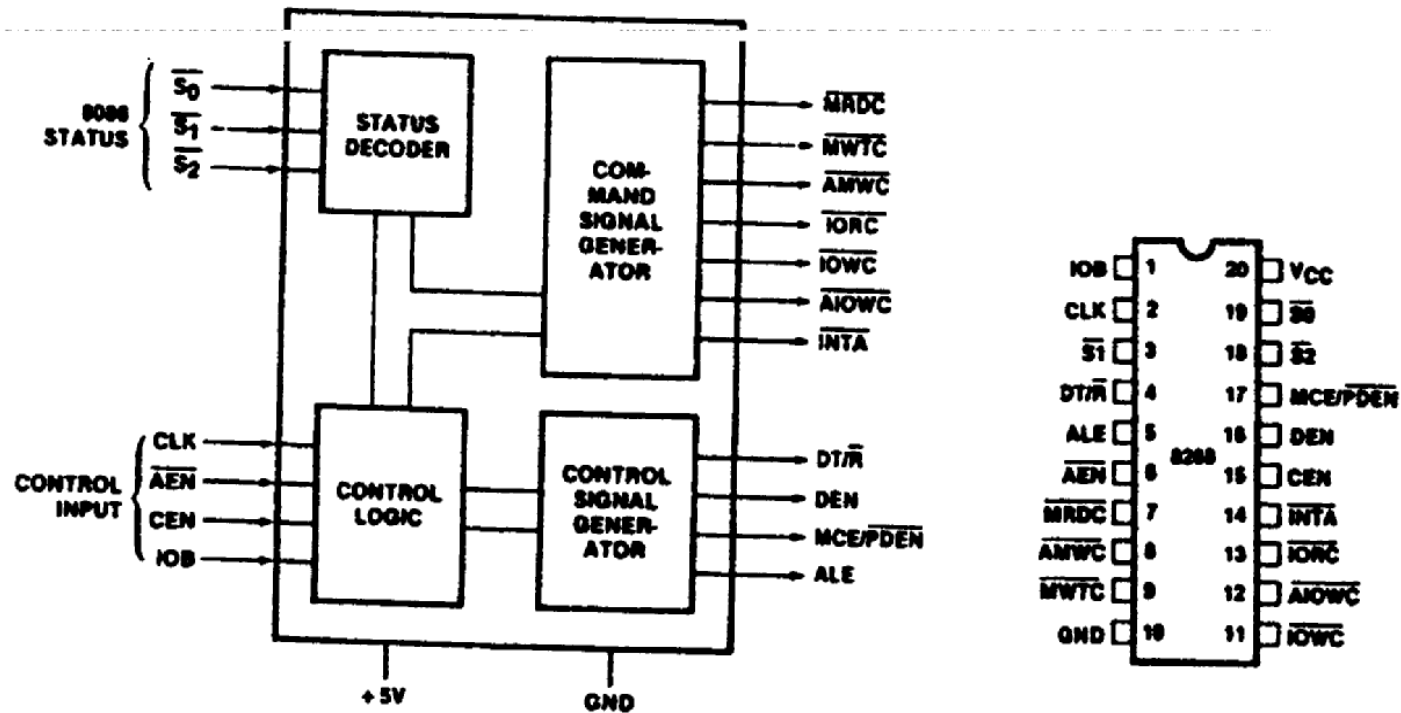



Block Diagram of the 8288

# Maximum Mode Interface

---

Status Inputs			CPU Cycle	8288 Command
$\overline{S2}$	$\overline{S1}$	$\overline{S0}$		
0	0	0	Interrupt Acknowledge	$\overline{INTA}$
0	0	1	Read I/O Port	$\overline{IORC}$
0	1	0	Write I/O Port	$\overline{IOWC}, \overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction Fetch	$\overline{MRDC}$
1	0	1	Read Memory	$\overline{MRDC}$
1	1	0	Write Memory	$\overline{MWTC}, \overline{AMWC}$
1	1	1	Passive	None

# Bus Cycle and Time States

  

# Bus Cycle and Time States

---

- A bus cycle defines the basic operation that a microprocessor performs to communicate with external devices
- Examples of bus cycles are memory read, memory write, input/output read and input/output write.
- A bus cycle corresponds to a sequence of events that starts with an address being output on the system bus followed by a read or write data transfer
- During these operations, a series of control signals are also produced by the MPU to control the direction and timing of the bus.
- Bus cycle consists of at least four clock periods, T1, T2, T3, and T4.
  - During T1 the MPU puts the address on the address bus
  - For a write memory cycle, data are put on the bus during state T2 and maintained thru T3 and T4.
  - When a read cycle is performed, the bus is first put in the high-Z state during T2 and data to be read must be available on the bus during T3 and T4.
  - Bus cycle duration of  $125 \text{ ns} \times 4 = 500 \text{ ns}$  in an 8 mhz 8088 system




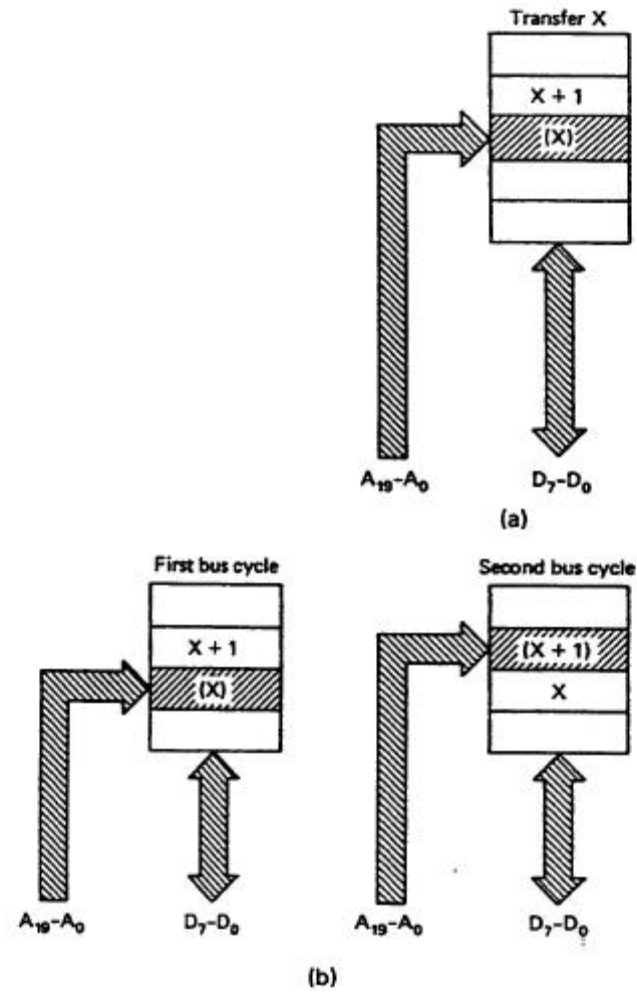
 



Figure 8-16 (a) Byte transfer by the 8088. (b) Word transfer by the 8088.

 

 


 

# Read Cycle of the 8088

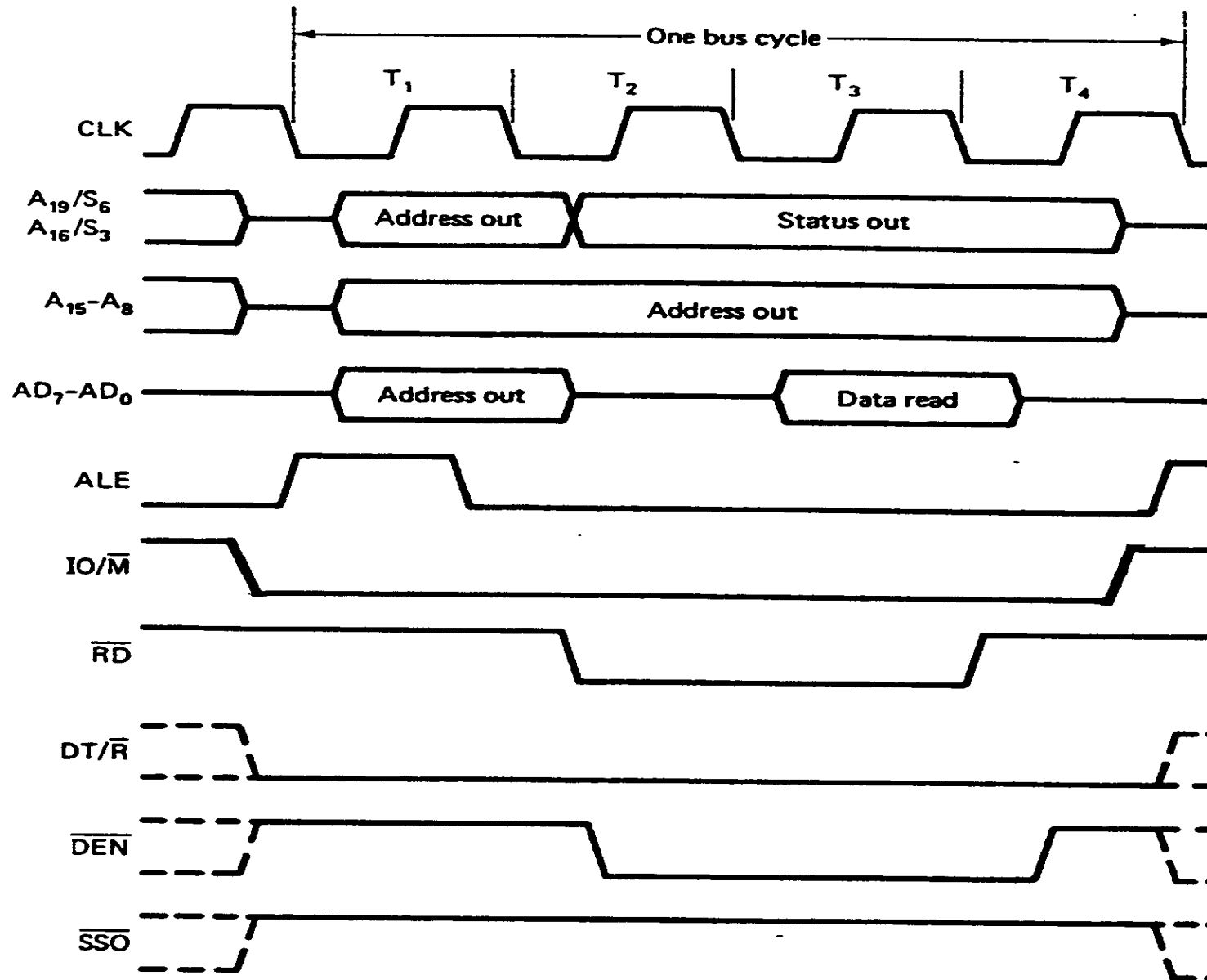


# Read Cycle of the 8086 - minimum mode

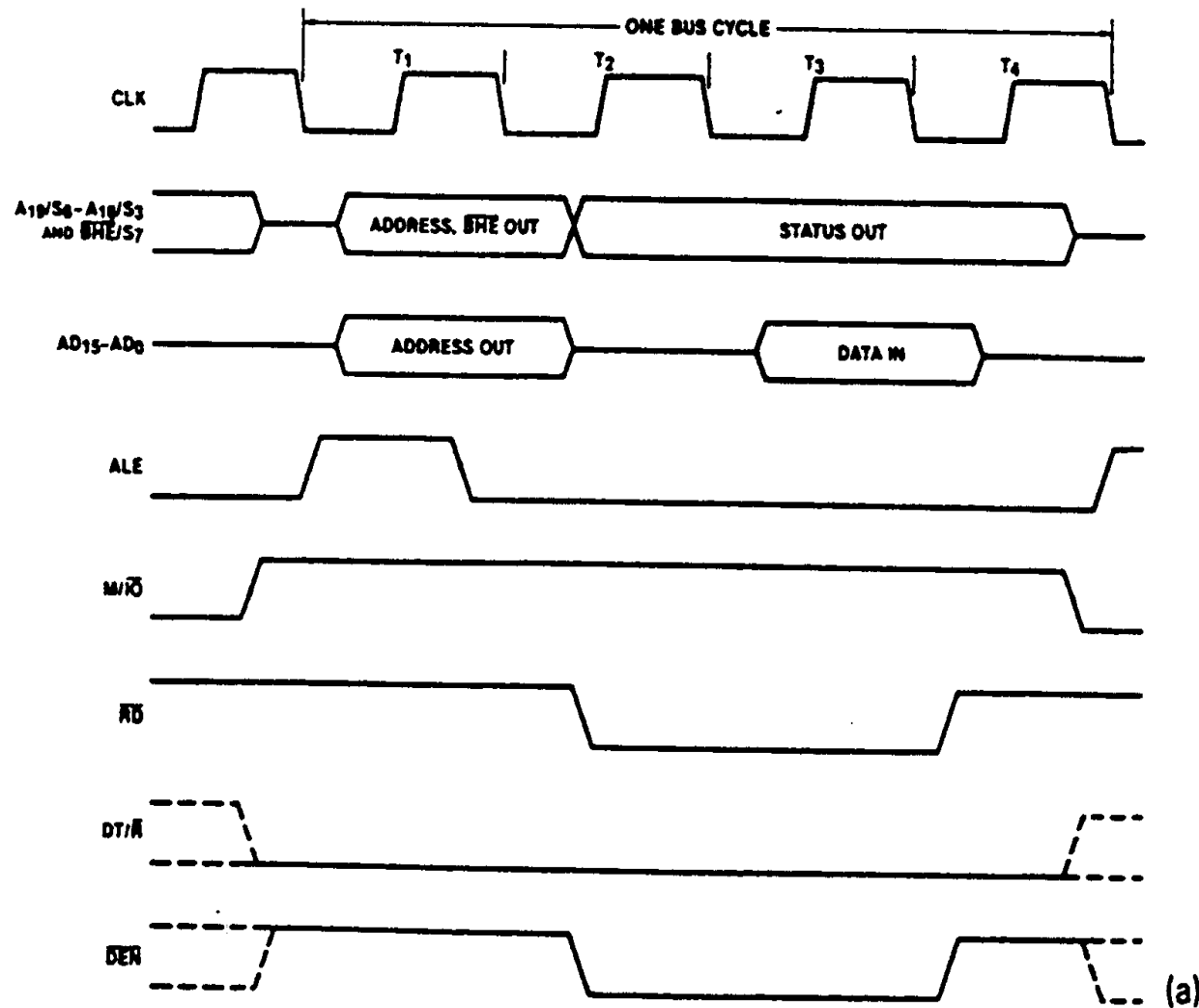


- BHE is output along with the address during T<sub>1</sub>
- Data can be read during T<sub>3</sub> over all 16 data bus lines
- $\overline{M/\overline{IO}}$  replaces IO/ $\overline{M}$
- $\overline{SSO}$  status signal is not produced

# Read Cycle of the 8086 - maximum mode


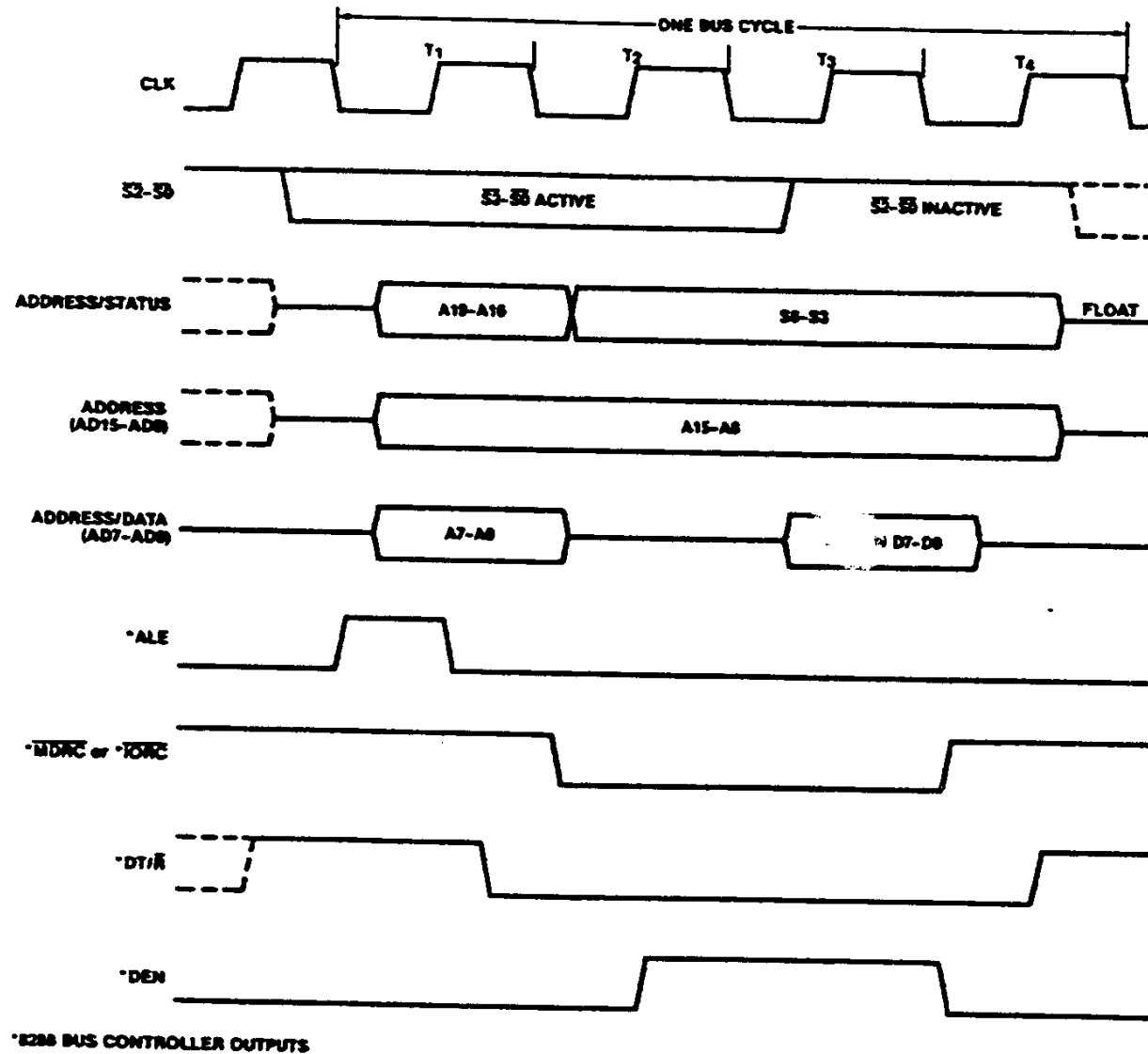


(b)

# Memory Interface

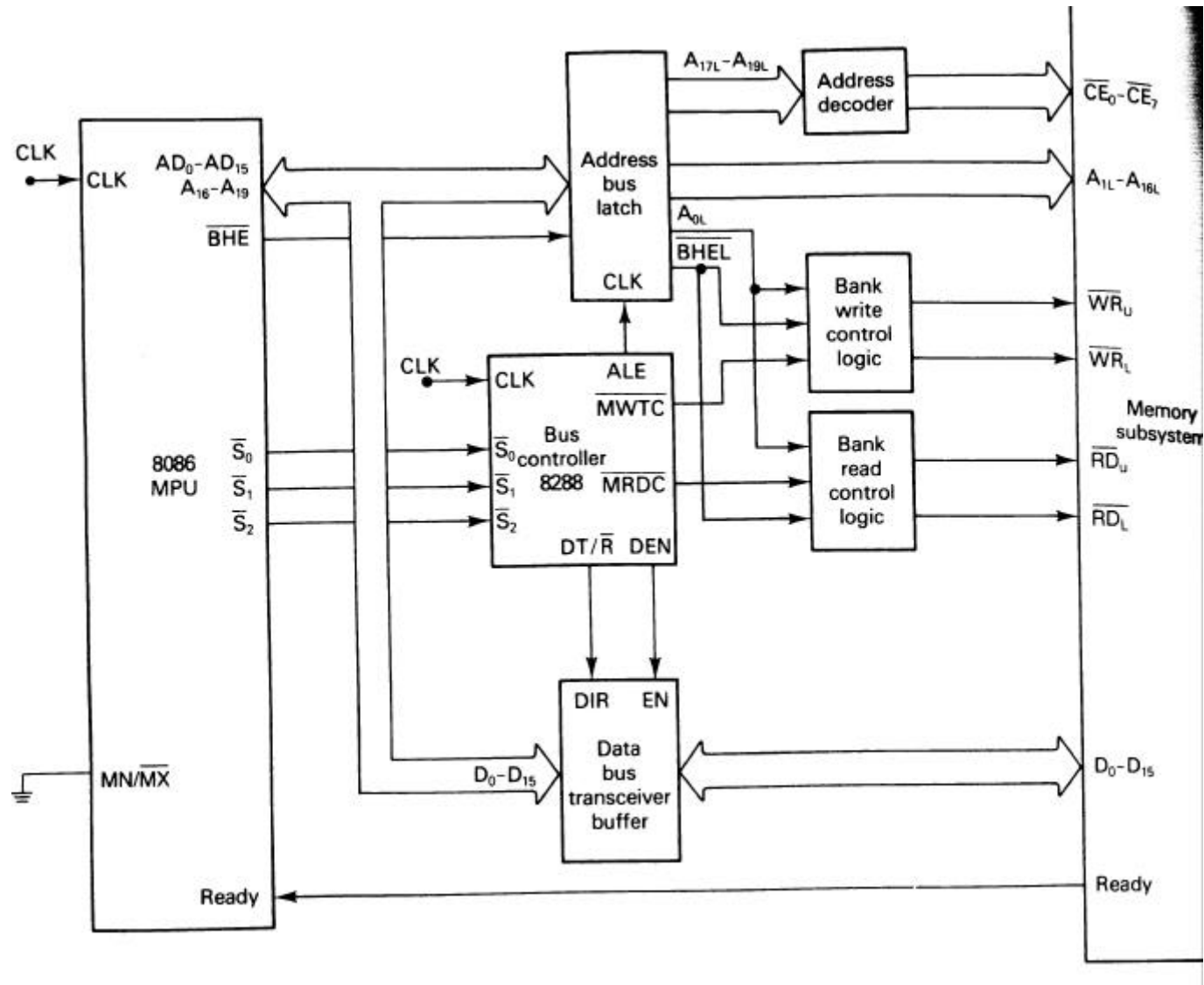


# Address Bus Latches and Buffers

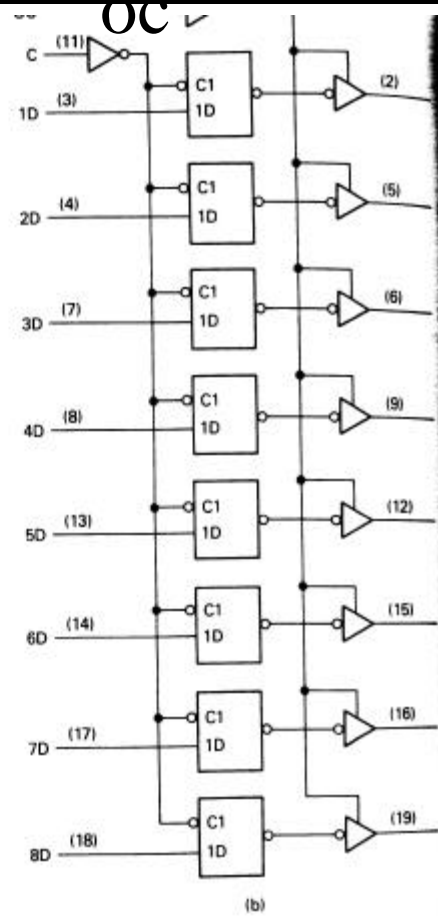 


Inputs			Output
$\overline{OC}$	Enable C	D	Q
L	H	H	H
L	H	L	L
L	L	X	$Q_c$
H	X	X	Z

(c)

# Address Latch Circuit

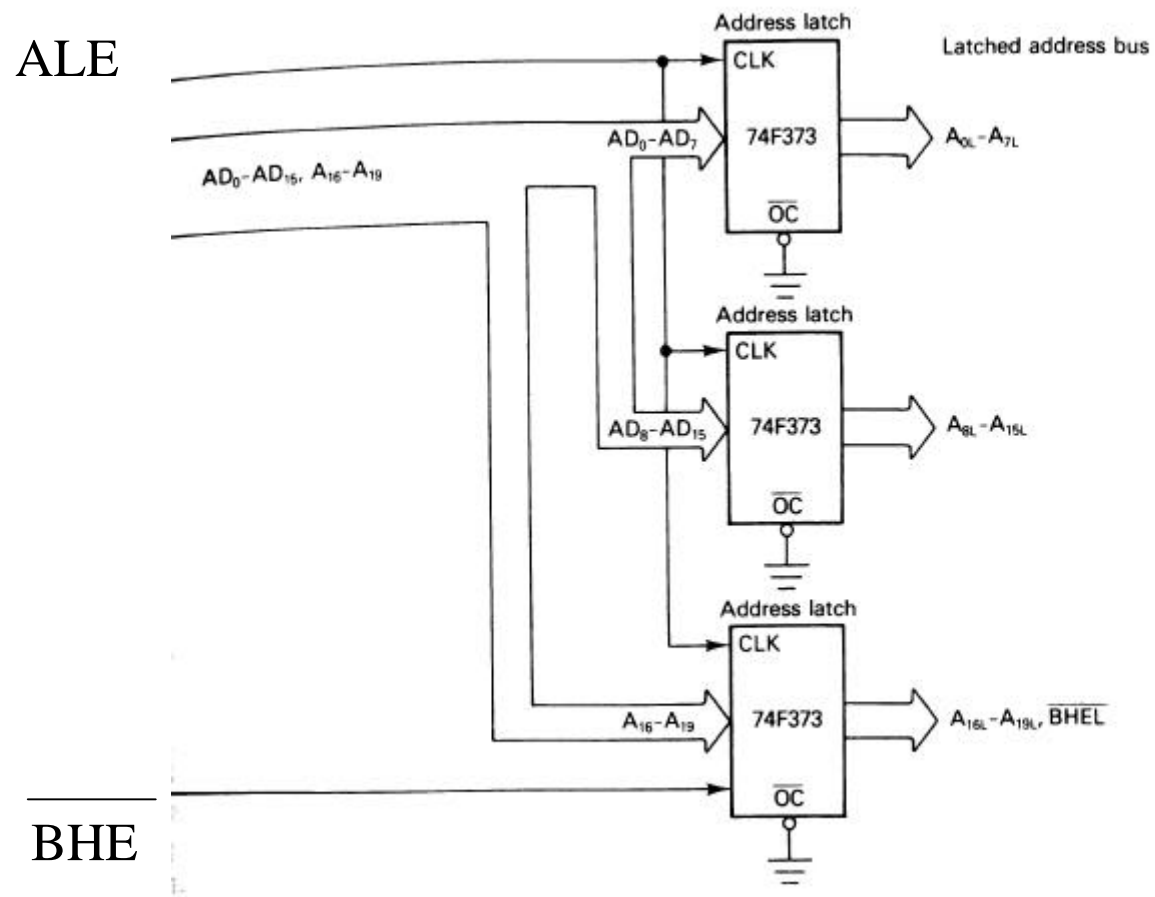

# Data Bus Transceiver Circuit

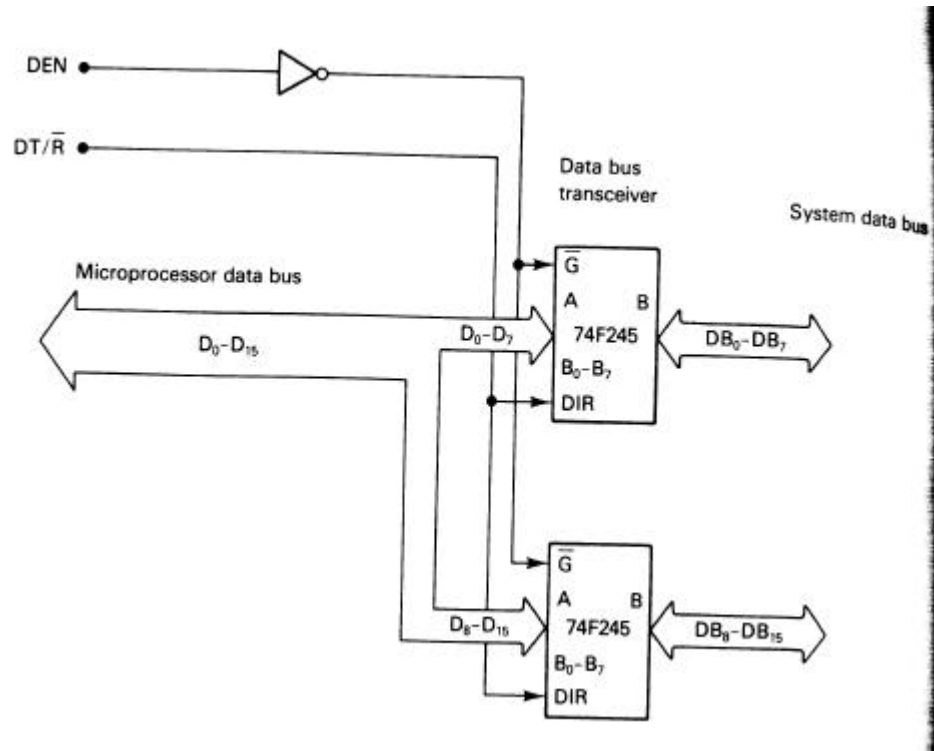

GBAR ENABLE	DIR	OPERATION
L	L	B data to A
L	H	A data to B
H	x	Isolation



# Buffered Systems

---

- Buffering (boosting) of the control, data, and address busses to provide sufficiently strong signals to drive various IC chips
  - When a pulse leaves an IC chip it can lose some of its strength depending on how far away the receiving IC is located
  - Plus the more pins a signal is connected to (i.e., fanout) the stronger the signal must be to drive them all which requires bus buffering
  - bus buffering = boosting the signals travelling on the busses
  - unidirectional bus 74LS244
  - bidirectional bus 74LS245

# 8088 system



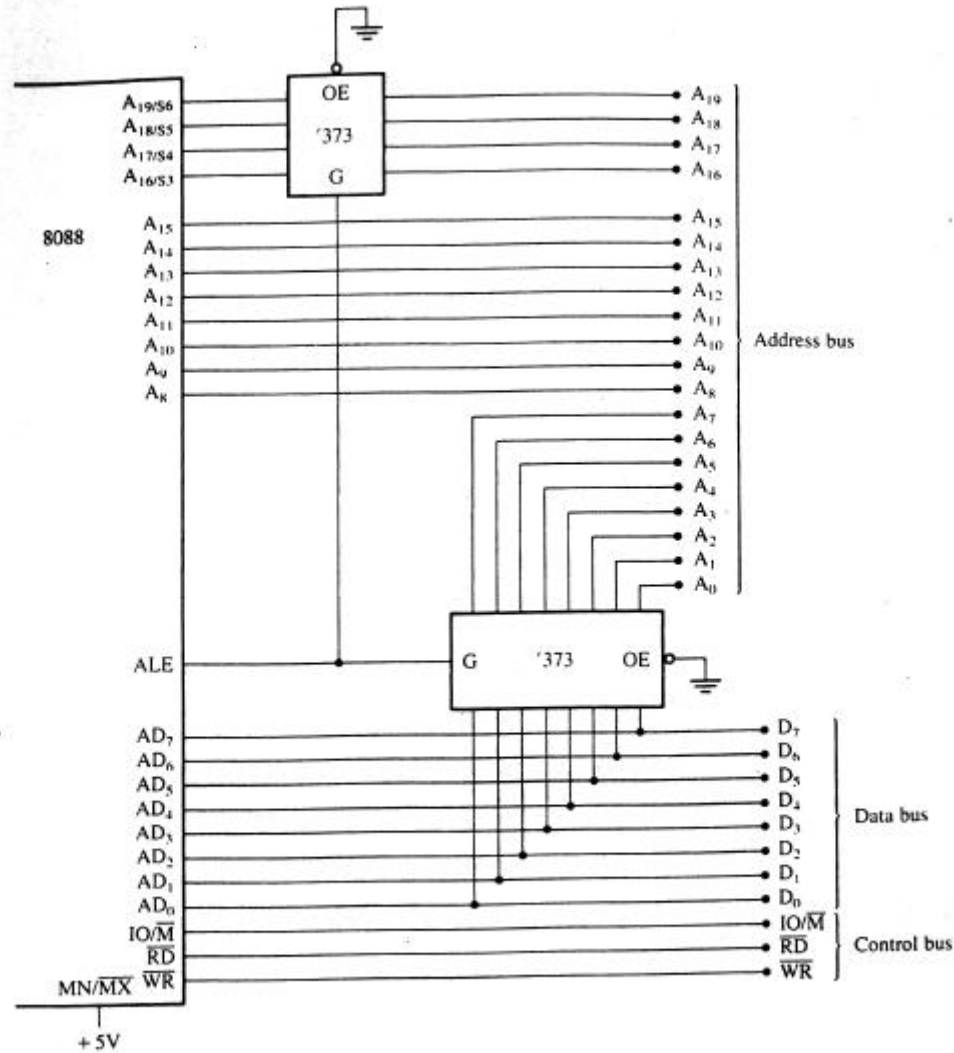


FIGURE 9-5 The 8088 microprocessor shown with a demultiplexed address bus. This is the model used to build many 8088-based systems.


# 8086 System

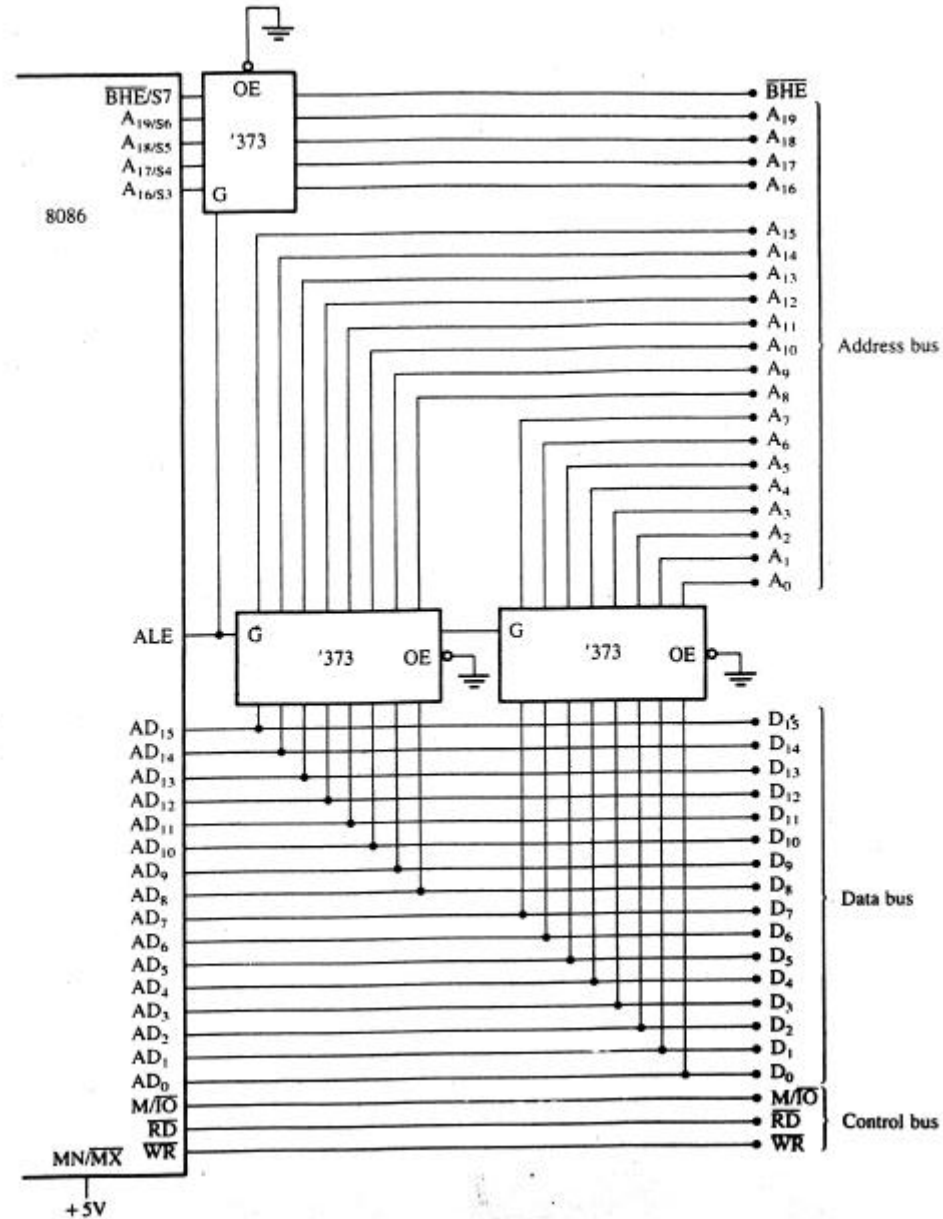

# Fully buffered 8088

 


# Fully Buffered 8086

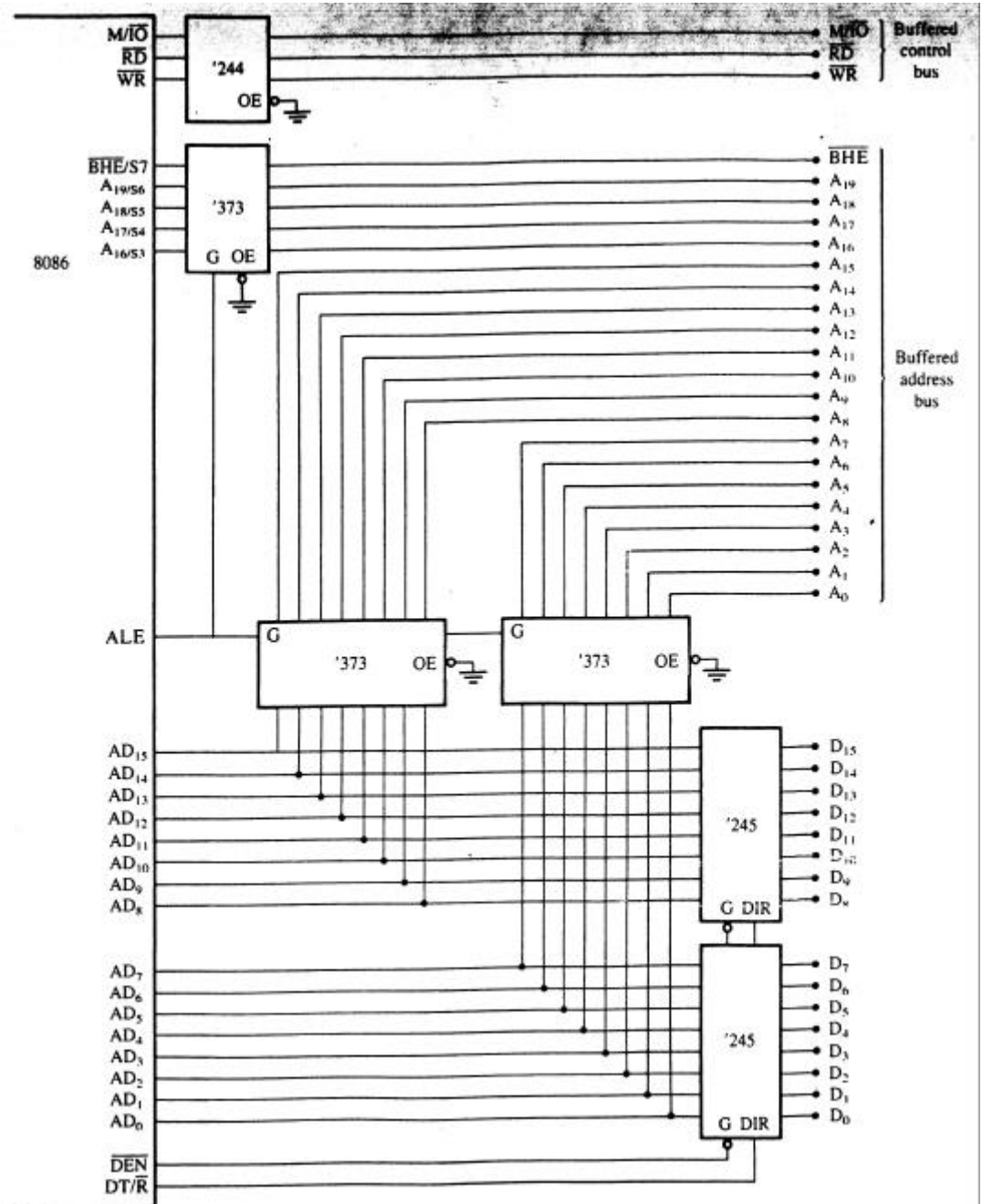


# Bank Write Control Logic

---

 


# Bank Read Control Logic

---

 



# Address Bus Configuration with Address Decoding

---

 




# 74F139 2-line to 4-line decoder

  

INPUTS			OUTPUTS			
ENABLE	SELECT		Y0	Y1	Y2	Y3
$\bar{G}$	B	A	Y0	Y1	Y2	Y3
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H	L	H
L	H	H	H	H	H	L

(c)

# Memory Interface - Again

 

# Address Decoder Circuit

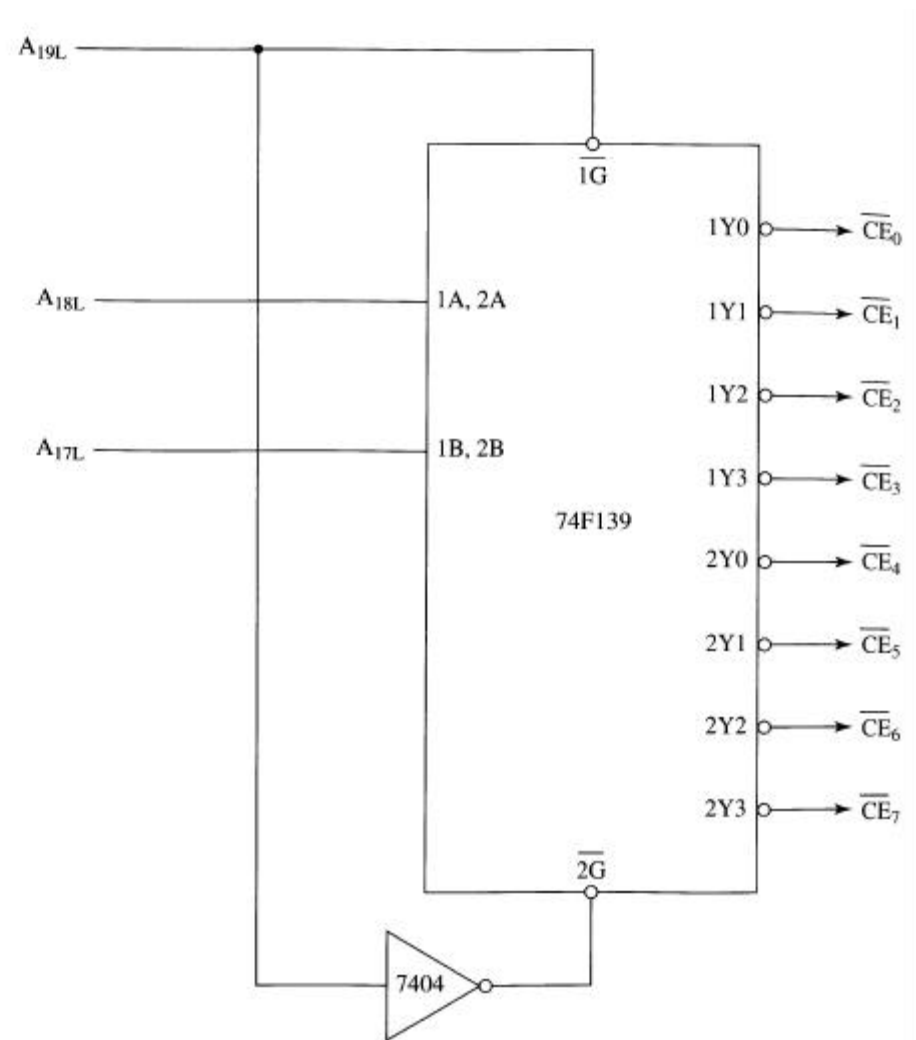


Figure 8-35 Address decoder circuit

# 8088 memory and address spaces

---


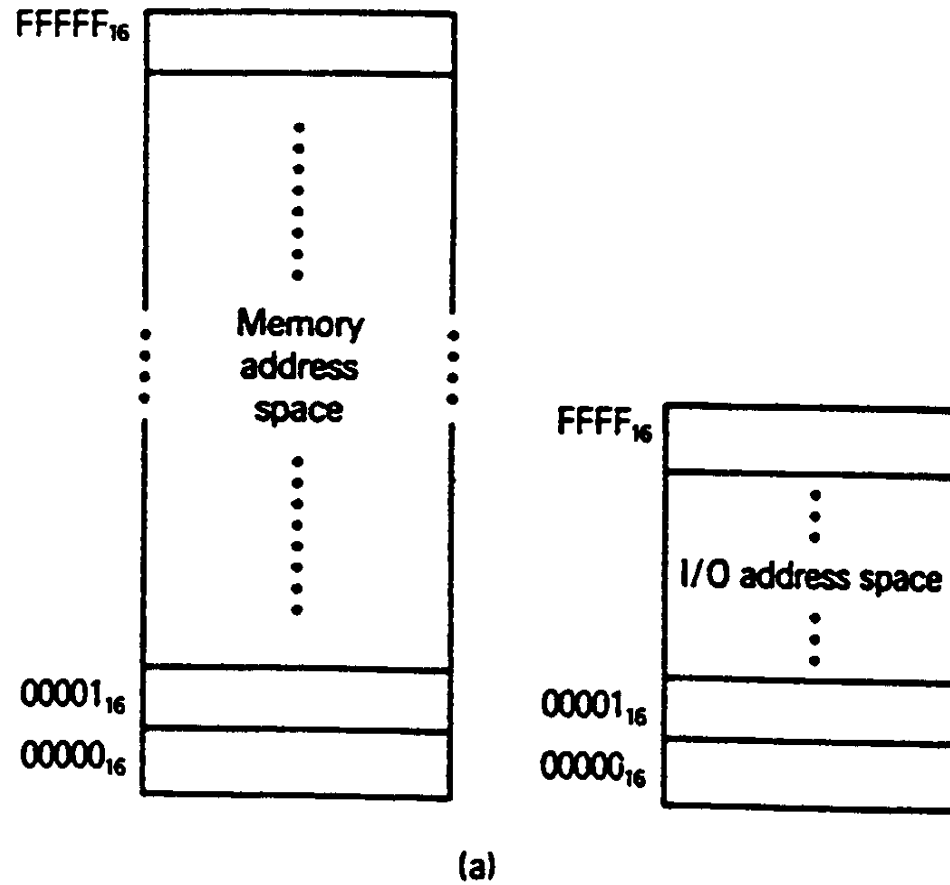


Figure 8-46 8088/8086 memory and I/O address spaces.

# Isolated I/O

 


I/O devices are treated separately from memory

Address 0000 to 00FF is referred to page 0. Special instructions exist for this address range


Byte wide ports

Word wide ports


# Memory Mapped I/O

 

# Maximum Mode I/O interface - 8088/8086

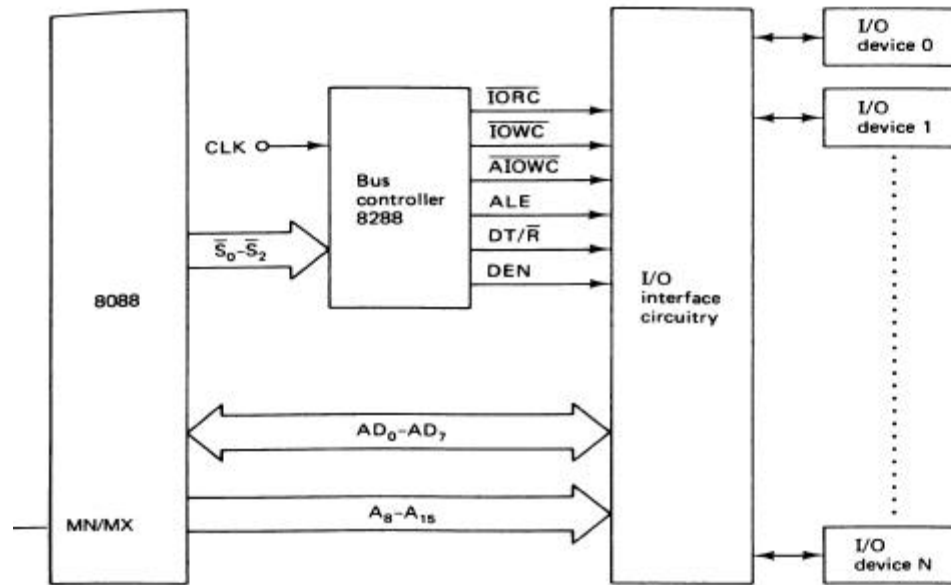

(a)

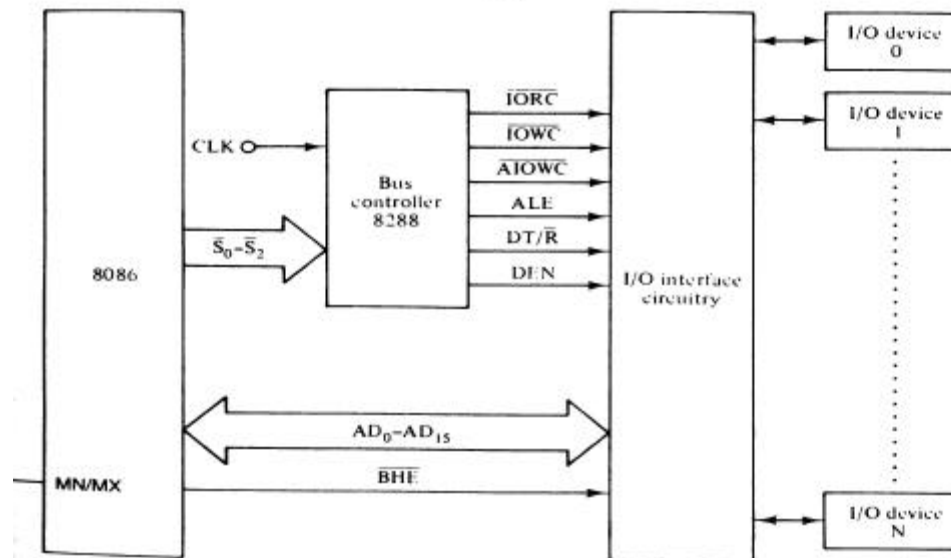

(b)

# I/O Bus Cycle Status Codes

---

Status inputs			CPU cycle	8288 command
$\bar{S}_2$	$\bar{S}_1$	$\bar{S}_0$		
0	0	0	Interrupt acknowledge	$\overline{INTA}$
0	0	1	Read I/O port	$\overline{IORC}$
0	1	0	Write I/O port	$\overline{IOWC}, \overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction fetch	$\overline{MRDC}$
1	0	1	Read memory	$\overline{MRDC}$
1	1	0	Write memory	$\overline{MWTC}, \overline{AMWC}$
1	1	1	Passive	None



# I/O Instructions

Mnemonic	Meaning	Format	Operation
IN	Input direct	IN Acc,Port	(Acc) ← (Port)      Acc = AL or AX
	Input indirect (variable)	IN Acc,DX	(Acc) ← ((DX))
OUT	Output direct	OUT Port,Acc	(Port) ← (Acc)
	Output indirect (variable)	OUT DX,Acc	((DX)) ← (Acc)

Example. Write a sequence of instructions that will output the data FFh to a byte wide output at address ABh of the I/O address space

```
MOV AL,0FFh
OUT 0ABh, AL
```

Example. Data is to be read from two byte wide input ports at addresses AAh and A9h and then this data will then be output to a word wide output port at address B00h

```
IN AL, 0AAh
MOV AH,AL
IN AL, 0A9h
MOV DX,0B00h
OUT DX,AX
```

# Input Bus Cycle of the 8088

 


Figure 8-52 Input bus cycle of the 8088.

# Output Bus Cycle of the 8088

 


Figure 8-53 Output bus cycle of the 8088.